



Digital Teknik II / Digital Design II

Dr. D. M. Akbar Hussain
Department of Electronic Systems

DE3 Course

1



Digital Teknik / Digital Design

Underviser: D. M. Akbar Hussain

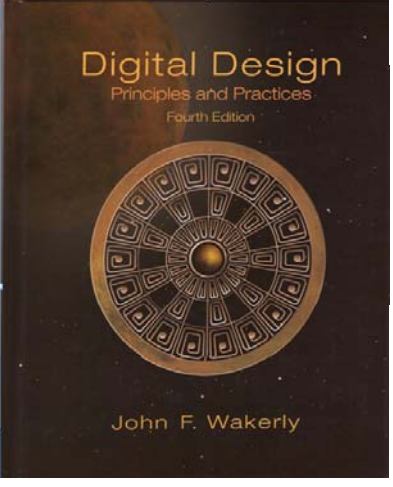

**Litteratur: Digital Design Principles & Practices
4th Edition by John F. Wakerly**

Dr. D. M. Akbar Hussain
Department of Electronic Systems

DE3 Course

2

Course Book




Digital Design
Principles and Practices
Fourth Edition
John F. Wakerly

Dr. D. M. Akbar Hussain
Department of Electronic Systems

DE3 Course

3

Course Web Page




<http://www.aue.auc.dk/~akbar/2010/Digital-Design-2-2010.html>

Dr. D. M. Akbar Hussain
Department of Electronic Systems

DE3 Course

4




Basic Aim (Hovedformålet)

To enable students to apply analysis, synthesis and implementation of basic digital circuits.

DE3 Course

Dr. D. M. Akbar Hussain
Department of Electronic Systems

5




Objective (Mål)

Students can make analysis and should be able to design digital circuits which is a central feature of data or electrical engineering.

DE3 Course

Dr. D. M. Akbar Hussain
Department of Electronic Systems

6




Course Contents (**Kursets Indhold**)

- Multi-vibrators & Sequential circuits.
- Bi-stable Circuits, Structure of Mono-stable and A-stable circuits.
- Modeling , Analysis and Synthesizing of circuits.
- Mealy and Moore State Machines there analysis, design and realization.
- Counters and Shift Registers.


DE3 Course

Dr. D. M. Akbar Hussain
Department of Electronic Systems

7




Digital Teknik / Digital Design




DE3 Course

Dr. D. M. Akbar Hussain
Department of Electronic Systems

8



Multivibrator Circuit




A circuit which is used to build most common two state systems, for example Oscillator, Timers and flip-flops.

- **Astable:** Circuit is not stable in either state and continuously oscillates from one state to the other and it does not require any input, for example clock etc.
- **Monostable:** Obviously as the name says it can have one stable state and one unstable state and it can flip into the unstable state for a determined period, but will eventually return to the stable state. Such a circuit is useful for creating a timing period of fixed duration in response to some external event. This circuit is also known as a one shot.
- **Bistable:** In such a circuit it will remain in one of the two states indefinitely. The circuit can be flipped from one state to the other by an external event or trigger. This type circuit is the fundamental building block of a register or memory device. This circuit is also known as a latch or a flip-flop.


DE3 Course

Dr. D. M. Akbar Hussain
Department of Electronic Systems

9




Multivibrator Circuit



DE3 Course

Dr. D. M. Akbar Hussain
Department of Electronic Systems

10



Sequential Circuit

Depend upon current input values as well as past sequence applied .


A circuit with n binary state variables can have 2^n possible states.

- Always Finite
- Never Infinite

DE3 Course

Dr. D. M. Akbar Hussain
Department of Electronic Systems

11



Some Basic Stuff

- What is a FSM
- It is a quintuple $(\Sigma, S, A, \delta, F)$, where:
- Σ input alphabet (a finite set of symbols)
- S finite set of states
- A an initial state, an element of S
- δ the state transition function: $\delta: S \times \Sigma \rightarrow S$
- F set of final states, a subset of S .

DE3 Course

Dr. D. M. Akbar Hussain
Department of Electronic Systems

12

Example

```
graph TD; idle((idle)) -- "no seat/-" --> idle; idle -- "seat/timer on" --> seated((seated)); seated -- "no seat/-" --> idle; seated -- "belt/-" --> belted((belted)); belted -- "no belt/timer on" --> seated; belted -- "belt/buzzer off" --> buzzer((buzzer)); buzzer -- "timer/buzzer on" --> idle; buzzer -- "no seat/buzzer off" --> idle;
```

Dr. D. M. Akbar Hussain
Department of Electronic Systems

DE3 Course 13

FSM Models

Mealy & Moore Models

Input Actions (State & Inputs)
Entry Actions (State)

Dr. D. M. Akbar Hussain
Department of Electronic Systems

DE3 Course 14

Structure of a State Machine

**Clocked Synchronous State Machine
(Mealy Machine)**

Next State = F (current state, input)
Output = G (current state, input)

Dr. D. M. Akbar Hussain
Department of Electronic Systems

DE3 Course 15

Structure of a State Machine

**Clocked Synchronous State Machine
(Moore Machine)**

Output = G (current state)

Dr. D. M. Akbar Hussain
Department of Electronic Systems

DE3 Course 16

Structure of a State Machine

Mealy Machine with Pipelined Outputs

Dr. D. M. Akbar Hussain
Department of Electronic Systems

DE3 Course 17


Instruction Pipeline

Instr. No.	Pipeline Stage						
	IF	ID	EX	MEM	WB		
1	IF	ID	EX	MEM	WB		
2		IF	ID	EX	MEM	WB	
3			IF	ID	EX	MEM	WB
4				IF	ID	EX	MEM
5					IF	ID	EX
Clock Cycle	1	2	3	4	5	6	7

Dr. D. M. Akbar Hussain
Department of Electronic Systems

DE3 Course 18

Various Instruction Pipelines




Micro-Architecture	Pipeline Stages
Intel P5 (Pentium)	5
Intel P6 (Pentium Pro)	14
Intel P6 (Pentium III)	10
IBM PowerPC 7	17
IBM Xenon	19
AMD Athlon	10
AMD Athlon XP	11
AMD Athlon64	12
AMD Phenom	12
AMD Opteron	15


Dr. D. M. Akbar Hussain
Department of Electronic Systems

DE3 Course 19

Characteristic Equation



Describing the function of a circuit:

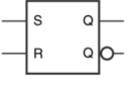

S	R	Q	QN
0	0	last Q	last QN
0	1	0	1
1	0	1	0
1	1	0	0


Device Type	Characteristic Equation
S-R latch	$Q^* = S + R' \cdot Q$
D latch	$Q^* = D$
Edge-triggered D flip-flop	$Q^* = D$
D flip-flop with enable	$Q^* = EN \cdot D + EN' \cdot Q$
Master/slave S-R flip-flop	$Q^* = S + R' \cdot Q$
Master/slave J-K flip-flop	$Q^* = J \cdot Q' + K' \cdot Q$
Edge-triggered J-K flip-flop	$Q^* = J \cdot Q' + K' \cdot Q$
T flip-flop	$Q^* = Q'$
T flip-flop with enable	$Q^* = EN \cdot Q' + EN' \cdot Q$

Dr. D. M. Akbar Hussain
Department of Electronic Systems

DE3 Course 20

Analysis

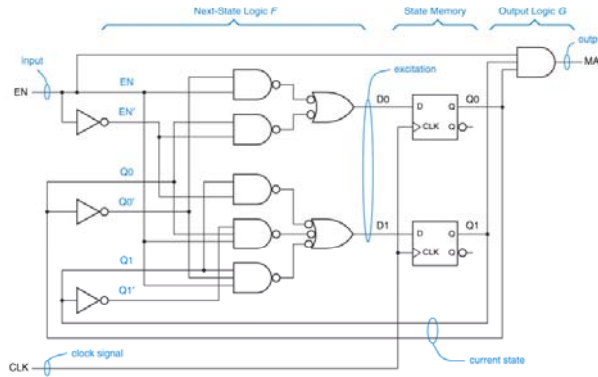Definition of a state machine:
 Next state = F (current state, input)
 Output = G (current state, input)



Dr. D. M. Akbar Hussain
 Department of Electronic Systems

Evaluation

		EN	
Q1 Q0	0	1	
00	00	01	
01	01	10	
10	10	11	
11	11	00	
		Q1* Q0*	

			EN		
S	0	1			
A	A	B			
B	B	C			
C	C	D			
D	D	A			
			S*		

			EN		
S	0	1			
A	A, 0	B, 0			
B	B, 0	C, 0			
C	C, 0	D, 0			
D	D, 0	A, 1			
			S*, MAX		

$$D0 = Q0 EN' + Q0' EN$$

$$D1 = Q1 EN' + Q1' Q0 EN + Q1 Q0' EN$$

Dr. D. M. Akbar Hussain
 Department of Electronic Systems

State Diagram

		EN	
S		0	1
A		A, 0	B, 0
B		B, 0	C, 0
C		C, 0	D, 0
D		D, 0	A, 1
		S*, MAX	

Dr. D. M. Akbar Hussain
Department of Electronic Systems


State/Output Table for Moore Machine Model


		EN		
S		0	1	MAXS
A		A	B	0
B		B	C	0
C		C	D	0
D		D	A	1
		S*		

		EN	
Q1 Q0		0	1
00		00	01
01		01	10
10		10	11
11		11	00
		Q1* Q0*	

Dr. D. M. Akbar Hussain
Department of Electronic Systems

State Diagram



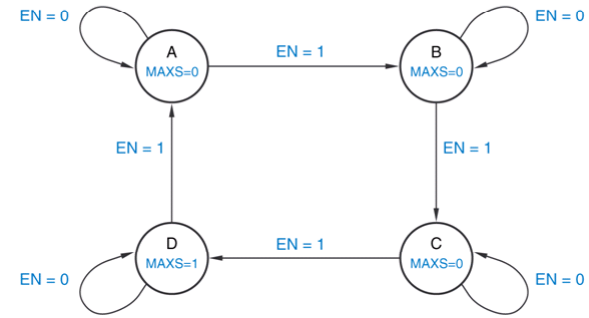


EN			
S	0	1	MAXS
A	A	B	0
B	B	C	0
C	C	D	0
D	D	A	1


S*			
EN			
Q1 Q0	0	1	
00	00	01	
01	01	10	
10	10	11	
11	11	00	

Dr. D. M. Akbar Hussain
Department of Electronic Systems

DE3 Course25

Modified/Redrawn Logic Diagram



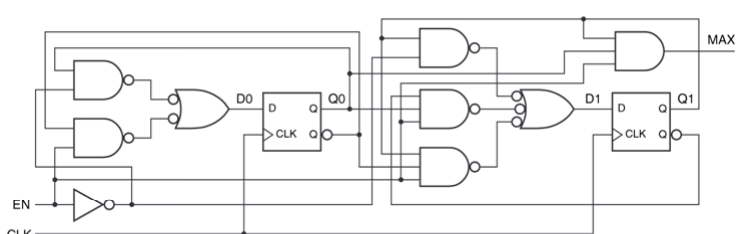

Dr. D. M. Akbar Hussain
Department of Electronic Systems

DE3 Course26




Timing Diagram

EN		
Q1 Q0	0	1
00	00	01
01	01	10
10	10	11
11	11	00
Q1* Q0*		

EN		
S	0	1
A	A, 0	B, 0
B	B, 0	C, 0
C	C, 0	D, 0
D	D, 0	A, 1
S*, MAX		

EN			
S	0	1	MAXS
A	A	B	0
B	B	C	0
C	C	D	0
D	D	A	1
S*			

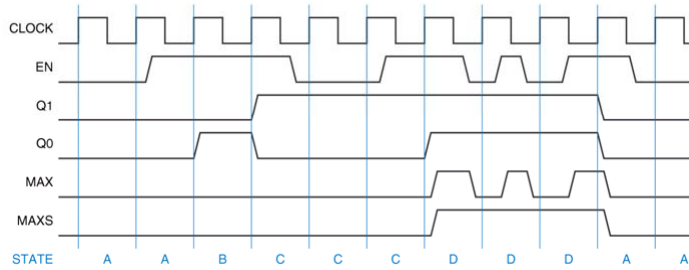

Dr. D. M. Akbar Hussain
Department of Electronic Systems



Summary

1. Determine the excitation equations for the flip-flops.
2. Substitute them into the characteristics equations to get the transition equations.
3. Use the transition equations to construct a transition table.
4. Determine the output equations.
5. Create a transition/output table.
6. Name the states.
7. Draw a state diagram.

Dr. D. M. Akbar Hussain
Department of Electronic Systems

State Machine with 3 Flip-flops & 8 states


Dr. D. M. Akbar Hussain
Department of Electronic Systems

Transition/Output & State/Output Table


(a)							(b)						
		XY							XY				
Q2	Q1	Q0	00	01	10	11	Z1Z2	S	00	01	10	11	Z1Z2
000	000	100	001	001	10			A	A	E	B	B	10
001	001	001	011	011	10			B	B	B	D	D	10
010	010	110	000	000	10			C	C	G	A	A	10
011	011	011	010	010	00			D	D	D	C	C	00
100	101	101	101	101	11			E	F	F	F	F	11
101	001	001	001	001	10			F	B	B	B	B	10
110	111	111	111	111	11			G	H	H	H	H	11
111	011	011	011	011	11			H	D	D	D	D	11
Q2* Q1* Q0*							S*						

Dr. D. M. Akbar Hussain
Department of Electronic Systems

State Diagram




S	XY	Z1	Z2
A	00	10	10
B	01	10	10
C	10	10	10
D	11	00	00
E	00	11	11
F	01	10	10
G	10	11	11
H	11	11	11

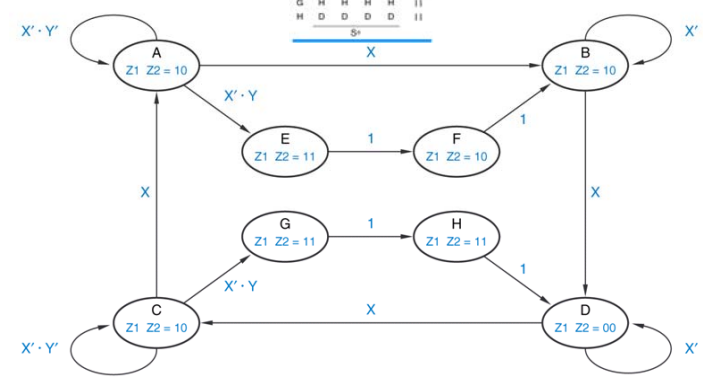

Dr. D. M. Akbar Hussain
Department of Electronic Systems

DE3 Course31


Designing a Clocked Synchronous State Machine



1. Construct a state / Output table.
2. If possible minimise the number of states.
3. Choose a set of state variable for state assignments.
4. Create a transition/output table by substituting state variable combinations into state/output table.
5. Select / Choose a flip flop, almost always it is D type flip flop.
6. Construct an excitation table, which shows the excitation values required to get to the next desired state for all possible state/input combinations.
7. Derive excitation equations from excitation table.
8. Derive output equations from the transition table.
9. Draw a logic diagram.

Dr. D. M. Akbar Hussain
Department of Electronic Systems


DE3 Course32



State Table Design


Design a clocked synchronous state machine with two inputs **A**, **B** and output **Z** so that **Z** is in state 1 if:

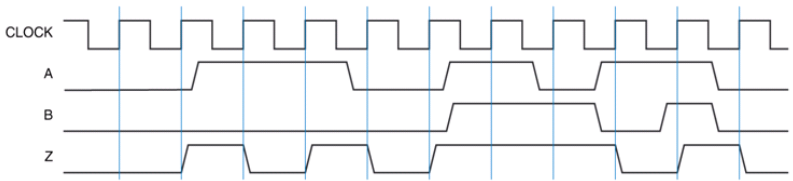A had the same value at each of the two previous clock ticks or **B** has been 1 since the last time the first condition was met/true otherwise, output should be 0.



Dr. D. M. Akbar Hussain
Department of Electronic Systems

DE3 Course 33



Design Steps

- From this verbal description create/construct a state / Output table.
- Minimise the number of states. The basic idea is that two or more states are equivalent if it is impossible to distinguish by observing the current and future output of the machine. Typically, these techniques are rarely used, because some time increasing the number of states simplifies the design, most engineers simplify the machine during state assignment (next step).


		A B					
Q1	Q2	Q3	00	01	11	10	Z
000	100	100	101	101	101	0	
100	110	110	101	101	0		
101	100	100	111	111	0		
110	110	110	111	101	1		
111	100	110	111	111	1		

		A B					
Q1	Q2	Q3	00	01	11	10	Z
A	B	B	C	C	0		
B	D	D	C	C	0		
C	B	B	E	E	0		
D	D	D	E	C	1		
E	B	D	E	E	1		

Dr. D. M. Akbar Hussain
Department of Electronic Systems

DE3 Course 34

Possible State Assignments




State Name	Assignment			
	Simplest Q1-Q3	Decomposed Q1-Q3	One-Hot Q1-Q5	Almost One-Hot Q1-Q4
INIT	000	000	00001	0000
A0	001	100	00010	0001
A1	010	101	00100	0010
OK0	011	110	01000	0100
OK1	100	111	10000	1000

Dr. D. M. Akbar Hussain
Department of Electronic Systems

DE3 Course 35

Disposition of States



- **Minimal Risk**
- **Minimal Cost**

Dr. D. M. Akbar Hussain
Department of Electronic Systems

DE3 Course 36

Timing Diagram & State Sequence

Dr. D. M. Akbar Hussain
Department of Electronic Systems

DE3 Course 37

Synthesis using D Type Flip-Flop


Q1 Q2 Q3	AB				Z
	00	01	11	10	
000	100	100	101	101	0
100	110	110	101	101	0
101	100	100	111	111	0
110	110	110	111	101	1
111	100	110	111	111	1

Q1* Q2* Q3*

Transition & Output Table

Dr. D. M. Akbar Hussain
Department of Electronic Systems

DE3 Course 38




State Machine

		AB					
Q1	Q2	Q3	00	01	11	10	Z
000	100	100	101	101	101	0	
100	110	110	101	101	101	0	
101	100	100	111	111	111	0	
110	110	110	111	101	101	1	
111	100	110	111	111	111	1	
		D1 D2 D3					

Excitation & Output Table


Dr. D. M. Akbar Hussain
Department of Electronic Systems

DE3 Course
39




Excitation Maps


		AB					
Q1	Q2	Q3	00	01	11	10	Z
000	100	100	101	101	101	0	
100	110	110	101	101	101	0	
101	100	100	111	111	111	0	
110	110	110	111	101	101	1	
111	100	110	111	111	111	1	
		D1 D2 D3					

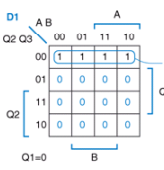

D1

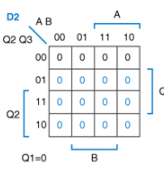

D2

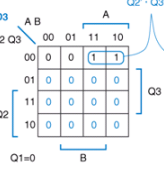

D3

$D1 = Q2' \cdot Q3' + Q1$
 $D2 = Q1 \cdot Q3' \cdot A' + Q1 \cdot Q3 \cdot A + Q1 \cdot Q2 \cdot B$
 $D3 = Q1 \cdot A + Q2' \cdot Q3' \cdot A$
 $Z = Q1 \cdot Q2 \cdot Q3' + Q1 \cdot Q2 \cdot Q3$
 $Z = Q1 \cdot Q2$

Dr. D. M. Akbar Hussain
Department of Electronic Systems

DE3 Course
40



1s-Counting Machine

Design a clocked synchronous state machine with 2 inputs X, Y and output Z. The output should be 1 if the number of inputs on X and Y since reset is a multiple of 4 and 0 otherwise.

Meaning	S	XY				Z
		00	01	11	10	
Got zero 1s (modulo 4)	S0	S0	S1	S2	S1	1
Got one 1 (modulo 4)	S1	S1	S2	S3	S2	0
Got two 1s (modulo 4)	S2	S2	S3	S0	S3	0
Got three 1s (modulo 4)	S3	S3	S0	S1	S0	0
S*						

Dr. D. M. Akbar Hussain
Department of Electronic Systems




Transition/Excitation & Output Table

Q1 Q2	XY				Z
	00	01	11	10	
00	00	01	11	01	1
01	01	11	10	11	0
11	11	10	00	10	0
10	10	00	01	00	0
Q1* Q2* or D1 D2					

Dr. D. M. Akbar Hussain
Department of Electronic Systems



Excitation Maps

 

$$D1 = Q2 \cdot X' \cdot Y + Q1' \cdot X \cdot Y + Q1 \cdot X' \cdot Y' + Q2 \cdot X \cdot Y'$$

$$D2 = Q1' \cdot X' \cdot Y + Q1' \cdot X \cdot Y' + Q2 \cdot X' \cdot Y' + Q2' \cdot X \cdot Y$$

$$Z = Q1' \cdot Q2'$$

		XY				Z
Q1	Q2	00	01	11	10	
00	00	01	11	01	1	
01	01	11	10	11	0	
11	11	10	00	10	0	
10	10	00	01	00	0	
		Q1* Q2* or D1 D2				

DE3 Course

Dr. D. M. Akbar Hussain
Department of Electronic Systems

43



State & Output Table for Combination-lock Machine


Meaning	S	X	
		0	1
Got zip	A	B, 01	A, 00
Got 0	B	B, 00	C, 01
Got 01	C	B, 00	D, 01
Got 011	D	E, 01	A, 00
Got 0110	E	B, 00	F, 01
Got 01101	F	B, 00	G, 01
Got 011011	G	E, 00	H, 01
Got 0110111	H	B, 11	A, 00
		S*, UNLK HINT	

DE3 Course

Dr. D. M. Akbar Hussain
Department of Electronic Systems

44

Transition/Excitation Table for Combination-lock Machine




Q1 Q2 Q3	X	
	0	1
000	001, 01	000, 00
001	001, 00	010, 01
010	001, 00	011, 01
011	100, 01	000, 00
100	001, 00	101, 01
101	001, 00	110, 01
110	100, 00	111, 01
111	001, 11	000, 00

Q1* Q2* Q3*, UNLK HINT

DE3 Course
Dr. D. M. Akbar Hussain
Department of Electronic Systems
45

Excitation Map



D1

X	Q1	X	
Q2 Q3	00	01	11 10
	00	0	0 1 0
	01	0	0 1 0
Q2	11	1	0 0 0
	10	0	1 1 0

Q1' · Q2 · Q3 · X' Q1 · Q2 · Q3'

D2

X	Q1	X	
Q2 Q3	00	01	11 10
	00	0	0 0 0
	01	0	0 1 1
Q2	11	0	0 0 0
	10	0	0 1 1

Q2' · Q3 · X Q2 · Q3' · X

D3

X	Q1	X	
Q2 Q3	00	01	11 10
	00	1	1 1 0
	01	1	1 0 0
Q2	11	0	1 0 0
	10	1	0 1 1

Q1' · Q2' · Q3' Q1 · Q3 · X'
Q1' · Q3' · X' Q2 · Q3' · X


D1 = Q1 · Q2' · X + Q1' · Q2 · Q3 + Q1 · Q2 · Q3'

D2 = Q2' · Q3 · X + Q2 · Q3' · X

D3 = Q1' · Q2' · Q3' + Q1 · Q3 · X' + Q2' · X' + Q3' · Q1' · X' + Q2 · Q3' · X

DE3 Course
Dr. D. M. Akbar Hussain
Department of Electronic Systems
46

Karnaugh Maps

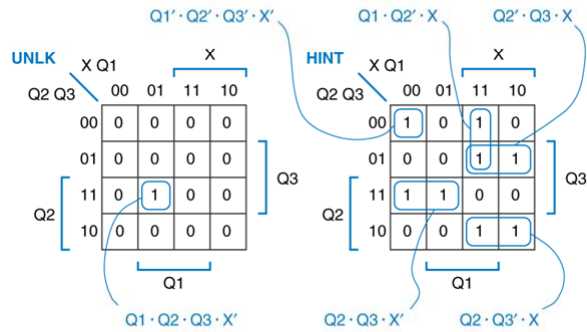

UNLK = $Q1 \cdot Q2 \cdot Q3 \cdot X'$

HINT = $Q1' \cdot Q2' \cdot Q3' \cdot X' + Q1 \cdot Q2' \cdot X + Q2' \cdot Q3 \cdot X + Q2 \cdot Q3 \cdot X' + Q2 \cdot Q3' \cdot X$

Spørgsmål Opgaver