



# CHAPTER 3

## Diodes

### Small Signal Model

#### Lecture # 2

### The Small Signal Model

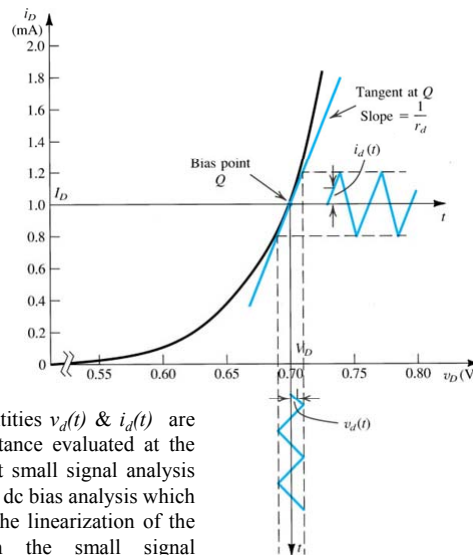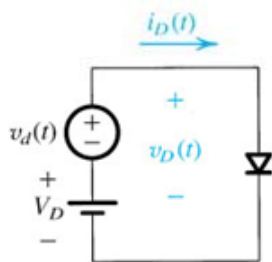


The superimposed small signal quantities  $v_d(t)$  &  $i_d(t)$  are related by diodes small signal resistance evaluated at the bias point and the conclusion is that small signal analysis can be performed separately from the dc bias analysis which is a big convenience resulted from the linearization of the diode characteristics inherent in the small signal approximation.
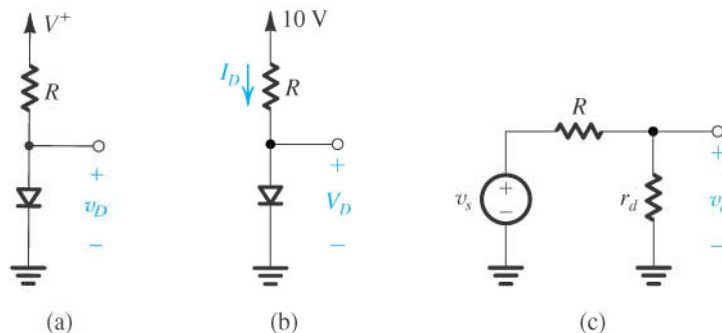
### Example 3.6



Consider the following circuit (a),  $V = 10\text{ V}$ ,  $R = 10\text{K}$ , a 60 Hz sinusoid of 1 V peak amplitude is superimposed, calculate the dc voltage of the diode and amplitude of the sine wave appearing across the diode, assuming the diode to have a 0.7 drop at 1 mA and  $n = 2$ .



$$I_D = \frac{V_{DD} - V_D}{R}$$

$$r_d = nV_T / I_D$$

$$v_d(\text{peak}) = v_s(\text{peak}) \frac{r_d}{R + r_d}$$

Figure 3.18 (a) Circuit for Example 3.6. (b) Circuit for calculating the dc operating point. (c) Small-signal equivalent circuit.

Dr. D. M. Akbar Hussain

Copyright © 2004 by Oxford University Press, Inc.


Department of Electronic Systems

3
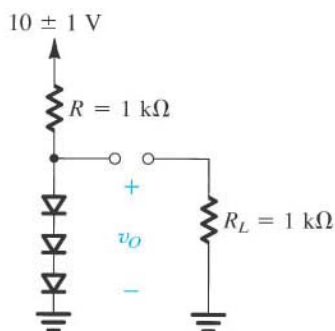
### Example 3.7 (Voltage Regulation)



Consider the following circuit, 3 diodes provide 2.1 V constant (regulated), calculate the percentage change in the regulated voltage by varying (a) 10 % change in supply voltage (b) connecting a 1 K load resistor, assuming  $n = 2$ .



$$I_D = \frac{V_{DD} - V_D}{R}$$

$$r_d = nV_T / I_D$$

$$r = r_{d1} + r_{d2} + r_{d3}$$

$$\Delta v_o = v_s(\text{peak}) \frac{r}{R + r}$$

Dr. D. M. Akbar Hussain

Copyright © 2004 by Oxford University Press, Inc.

Department of Electronic Systems

4

### Exercise 3.14



Find the value of the diode small signal resistance at a bias current of 0.1 mA, 1 mA and 10 mA, assume  $n = 1$ .

$$r_d = nV_T / I_D$$

Dr. D. M. Akbar Hussain

Copyright © 2004 by Oxford University Press, Inc.

Department of Electronic Systems

5

### Exercises 3.15



Consider a diode with  $n = 2$  biased at 1 mA, find the change in current as a result of changing the voltage by;

- (a) -20 mV
- (b) -10 mV
- (c) -5 mV
- (d) +5 mV
- (e) +10 mV
- (f) +20 mV

For each case do the calculations using

- (i) Small signal model
- (ii) Exponential mode.

Small Signal Model

$$i_D = I_D + i_d$$

$$i_d = \frac{I_D}{nV_T} v_d$$

$$i_D = I_S e^{\frac{v_d}{nV_T}}$$

Exponential Model

Dr. D. M. Akbar Hussain

Copyright © 2004 by Oxford University Press, Inc.


Department of Electronic Systems

6
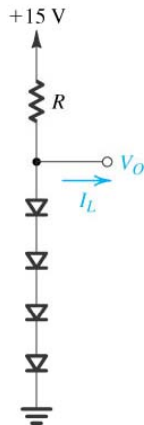
### Exercises 3.16



Design the following circuit so that  $V_O = 3\text{ V}$ , when  $I_L = 0$  and  $V_O$  changes by  $40\text{ mV}$  per  $1\text{ mA}$  of load current. Find the value of  $R$  and the junction area of each diode (assume all four diodes are identical) relative to a diode of  $0.7\text{ V}$  drop at  $1\text{ mA}$ , assume  $n = 1$ .



$$\frac{\Delta v}{\Delta i} = \frac{40\text{ mV}}{1\text{ mA}} = ?$$

$$r_d = \frac{1}{4}$$

$$I_D = nV_T / r_d$$

$$I_D = I_S e^{v_d / nV_T}$$

$$\frac{I_{D2}}{I_{D1}} = \frac{I_{S2}}{I_{S1}} e^{\Delta v / nV_T}$$


Dr. D. M. Akbar Hussain

Copyright © 2004 by Oxford University Press, Inc.



Department of Electronic Systems

7


### Summary of Diode Modelling

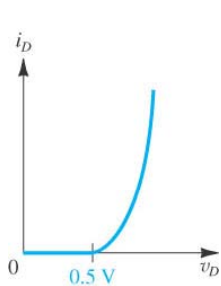


Exponential

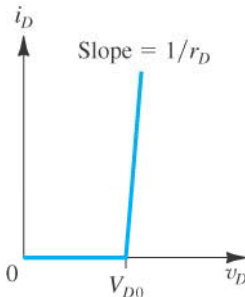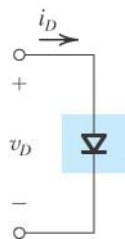


Piecewise Linear

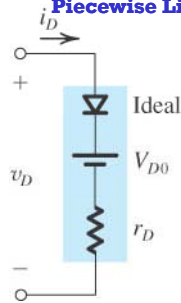

Dr. D. M. Akbar Hussain

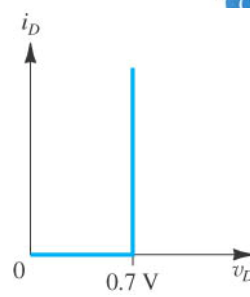

Constant Voltage Drop

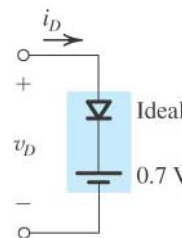


Department of Electronic Systems


Copyright © 2004 by Oxford University Press, Inc.

8



## Summary

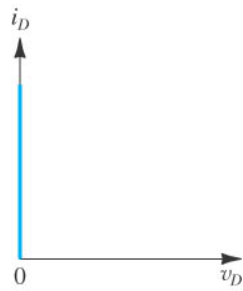

Ideal Diode Model

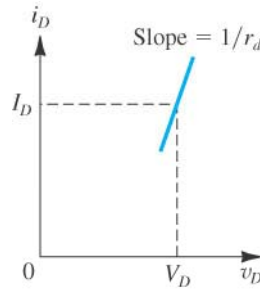

Small Signal Model

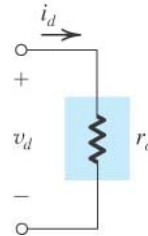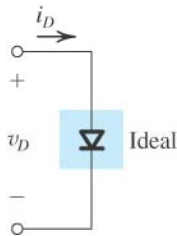

Copyright © 2004 by Oxford University Press, Inc.

Dr. D. M. Akbar Hussain  
Department of Electronic Systems

9

## Voltage Regulation (Breakdown Region)




Copyright © 2004 by Oxford University Press, Inc.

Dr. D. M. Akbar Hussain  
Department of Electronic Systems

10

## Zener Diode Characteristics

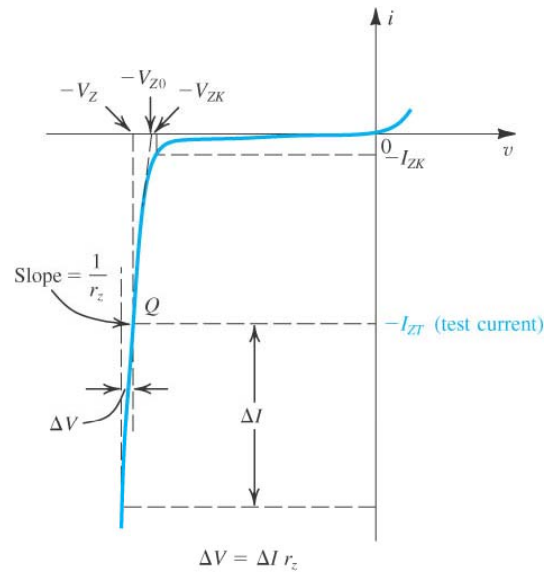


Dr. D. M. Akbar Hussain

Copyright © 2004 by Oxford University Press, Inc.

Department of Electronic Systems


11

## Zener Diode Modelling

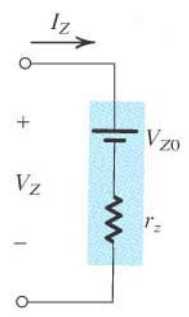

$$V_Z = V_{Z0} + r_z I_Z$$
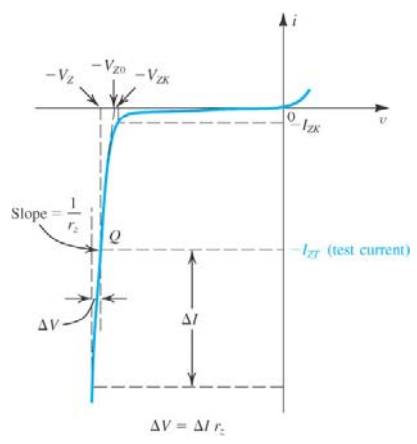
$$I_Z > I_{ZK} \text{ and } V_Z > V_{Z0}$$



Dr. D. M. Akbar Hussain

Copyright © 2004 by Oxford University Press, Inc.

Department of Electronic Systems

12


### Example 3.8

$V_Z = 6.8$  V at  $I_Z = 5$  mA,  $r_Z = 20$  ohm and  $I_{ZK} = 0.2$  mA, supply voltage is 10 V but can vary by  $\pm 1$  V.

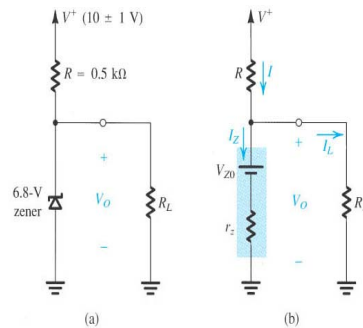1. Find  $V_O$  with no load and supply voltage 10 V.
2. Find the change in  $V_O$  resulting from  $\pm 1$  V change. Note that  $(\Delta V_O / \Delta V)$  usually expressed in mV/v as line regulation.
3. Find the change in  $V_O$  resulting from connecting load resistance  $R_L$  that draws  $I_L = 1$  mA, hence find the load regulation  $(\Delta V_O / \Delta I_L)$  in mV/mA.
4. Find the change in  $V_O$  when  $R_L = 2$  K $\Omega$ .
5. Find the change in  $V_O$  when  $R_L = 5$  K $\Omega$ .
6. What is the maximum value  $R_L$  for which the diode still operate in the breakdown region ?

$$V_Z = V_{Z0} + r_Z I_Z$$

$$I_Z > I_{ZK} \text{ and } V_Z > V_{Z0}$$



Dr. D. M. Akbar Hussain

Copyright © 2004 by Oxford University Press, Inc.

Department of Electronic Systems

13

### Exercises 3.17, 3.18 & 3.19



#### EXERCISES

- ✓ 3.17 A zener diode whose nominal voltage is 10 V at 10 mA has an incremental resistance of 50  $\Omega$ . What voltage do you expect if the diode current is halved? Doubled? What is the value of  $V_{Z0}$  in the zener model?  
 Ans. 9.75 V; 10.5 V; 9.5 V
- ✓ D3.18 A zener diode exhibits a constant voltage of 5.6 V for currents greater than five times the knee current.  $I_{ZK}$  is specified to be 1 mA. The zener is to be used in the design of a shunt regulator fed from a 15-V supply. The load current varies over the range of 0 mA to 15 mA. Find a suitable value for the resistor  $R$ . What is the maximum power dissipation of the zener diode?  
 Ans. 470  $\Omega$ ; 112 mW
- 3.19 A shunt regulator utilizes a zener diode whose voltage is 5.1 V at a current of 50 mA and whose incremental resistance is 7  $\Omega$ . The diode is fed from a supply of 15-V nominal voltage through a 200- $\Omega$  resistor. What is the output voltage at no load? Find the line regulation and the load regulation.  
 Ans. 5.1 V; 33.8 mV/V; -7 mV/mA


Dr. D. M. Akbar Hussain

Copyright © 2004 by Oxford University Press, Inc.

Department of Electronic Systems

14

# Rectifier Circuits

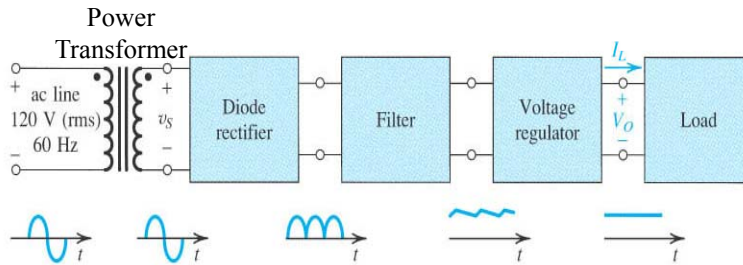


Dr. D. M. Akbar Hussain

Copyright © 2004 by Oxford University Press, Inc.


Department of Electronic Systems

15


# Half Wave Rectifier

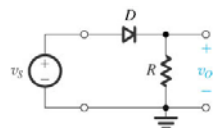


(a)

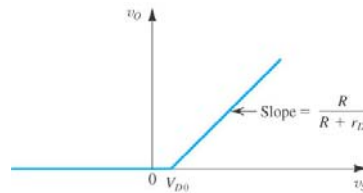

(c)

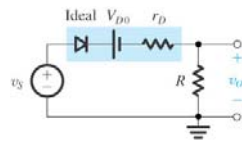

(b)

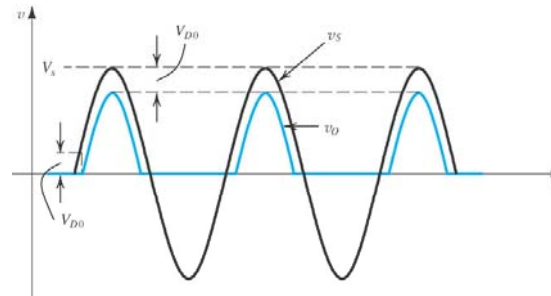

(d)

$$v_o = 0, v_s < V_{D0}$$

$$v_o = (v_s - V_{D0}) (R / (R + r_D)), v_s \geq V_{D0}$$

$$v_o \approx v_s - V_{D0} \text{ because } r_D \ll R$$

Dr. D. M. Akbar Hussain


Copyright © 2004 by Oxford University Press, Inc.

Department of Electronic Systems

16



### Exercise: 3.20

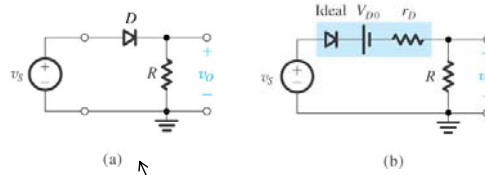

#### EXERCISE

3.20 For the half-wave rectifier circuit in Fig. 3.25(a), neglecting the effect of  $r_D$ , show the following: (a) For the half-cycles during which the diode conducts, conduction begins at an angle  $\theta = \sin^{-1}(V_{D0}/V_s)$  and terminates at  $(\pi - \theta)$ , for a total conduction angle of  $(\pi - 2\theta)$ . (b) The average value (dc component) of  $v_O$  is  $V_O \approx (1/\pi)V_s - V_{D0}/2$ . (c) The peak diode current is  $(V_s - V_{D0})/R$ .

Find numerical values for these quantities for the case of 12-V (rms) sinusoidal input,  $V_{D0} = 0.7$  V, and  $R = 100 \Omega$ . Also, give the value for PIV.

Ans. (a)  $\theta = 2.4^\circ$ , conduction angle =  $175^\circ$ ; (b) 5.05 V; (c) 163 mA; 17 V

Dr. D. M. Akbar Hussain

Copyright © 2004 by Oxford University Press, Inc.

Department of Electronic Systems

17

### Full Wave Rectifier

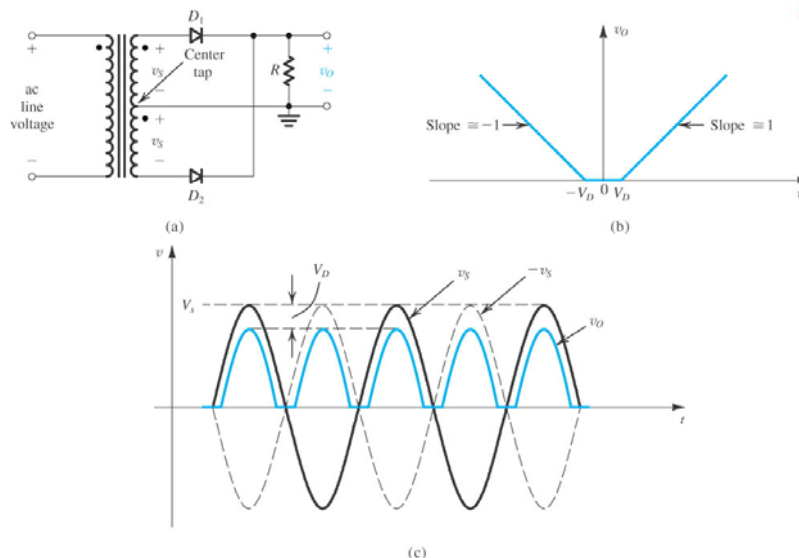


Figure 3.26 Full-wave rectifier utilizing a transformer with a center-tapped secondary winding: (a) circuit; (b) transfer characteristic assuming a constant-voltage-drop model for the diodes; (c) input and output waveforms.


Dr. D. M. Akbar Hussain

Copyright © 2004 by Oxford University Press, Inc.

Department of Electronic Systems

18

### Exercise 3.21

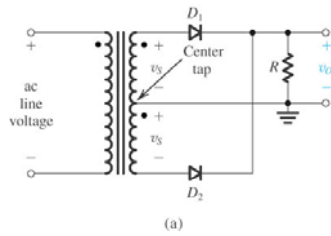

#### EXERCISE

3.21 For the full-wave rectifier circuit in Fig. 3.26(a), neglecting the effect of  $r_D$ , show the following: (a) The output is zero for an angle of  $2 \sin^{-1}(V_D/V_s)$  centered around the zero-crossing points of the sine-wave input. (b) The average value (dc component) of  $v_o$  is  $V_O \approx (2/\pi)V_s - V_D$ . (c) The peak current through each diode is  $(V_s - V_D)/R$ . Find the fraction (percentage) of each cycle during which  $v_o > 0$ , the value of  $V_O$ , the peak diode current, and the value of PIV, all for the case in which  $v_s$  is a 12-V (rms) sinusoid,  $V_D \approx 0.7$  V, and  $R = 100 \Omega$ .

Ans. 97.4%; 10.1 V; 163 mA; 33.2 V

### Bridge Rectifier


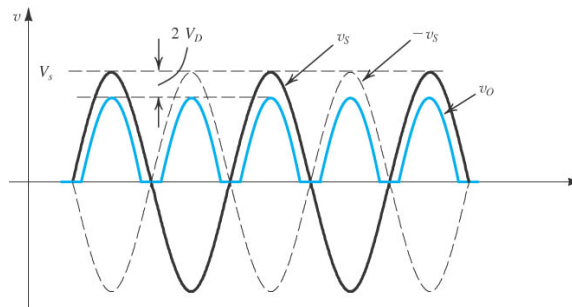
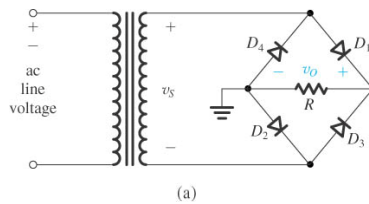


Figure 3.27 The bridge rectifier. (a) circuit, (b) input and output waveforms.

## Exercise 3.22

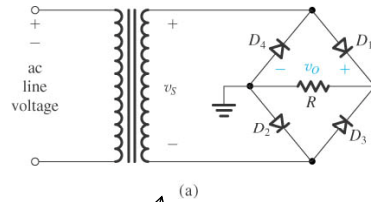

(a)

### EXERCISE

3.22 For the bridge rectifier circuit of Fig. 3.27(a), use the constant-voltage-drop diode model to show that (a) the average (or dc component) of the output voltage is  $V_O = (2/\pi)V_s - 2V_D$  and (b) the peak diode current is  $(V_s - 2V_D)/R$ . Find numerical values for the quantities in (a) and (b) and the PIV for the case in which  $v_s$  is a 12-V (rms) sinusoid,  $V_D = 0.7$  V, and  $R = 100 \Omega$ .

Ans. 9.4 V; 156 mA; 16.3 V


Dr. D. M. Akbar Hussain

Copyright © 2004 by Oxford University Press, Inc.


Department of Electronic Systems

21

## Capacitor Filter

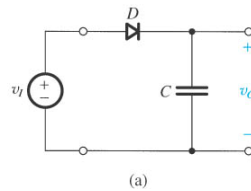

(a)

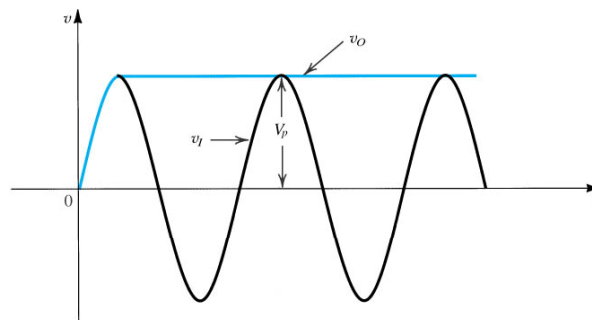

(b)

Figure 3.28 (a) A simple circuit used to illustrate the effect of a filter capacitor. (b) Input and output waveforms assuming an ideal diode. Note that the circuit provides a dc voltage equal to the peak of the input sine wave. The circuit is therefore known as a peak rectifier or a peak detector.

Dr. D. M. Akbar Hussain

Copyright © 2004 by Oxford University Press, Inc.

Department of Electronic Systems

22

## Capacitor Filter (Realistic Situation)

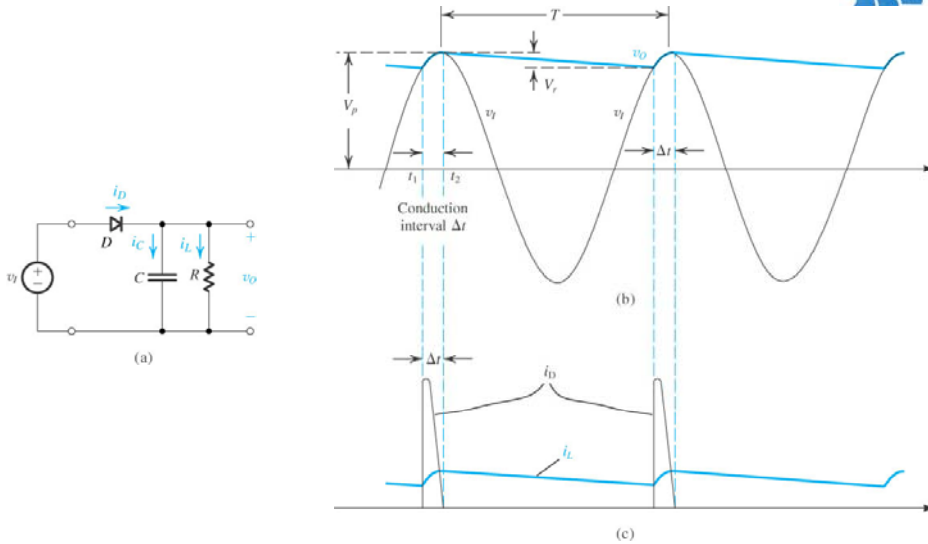


Figure 3.29 Voltage and current waveforms in the peak rectifier circuit with  $CR \ll T$ . The diode is assumed ideal.

Dr. D. M. Akbar Hussain

Copyright © 2004 by Oxford University Press, Inc.

Department of Electronic Systems

23

## Full Wave Peak Rectifier

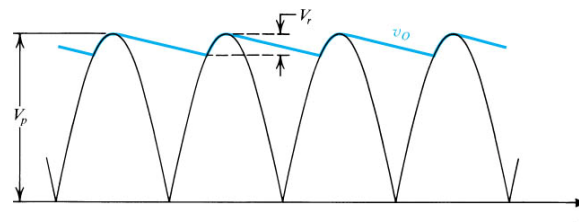


Figure 3.30 Waveforms in the full-wave peak rectifier.

Dr. D. M. Akbar Hussain

Copyright © 2004 by Oxford University Press, Inc.

Department of Electronic Systems

24

## Exercise 3.24



D3.24 Consider a bridge-rectifier circuit with a filter capacitor  $C$  placed across the load resistor  $R$  for the case in which the transformer secondary delivers a sinusoid of 12 V (rms) having a 60-Hz frequency and assuming  $V_D = 0.8$  V and a load resistance  $R = 100 \Omega$ . Find the value of  $C$  that results in a ripple voltage no larger than 1 V peak-to-peak. What is the dc voltage at the output? Find the load current. Find the diodes' conduction angle. What is the average diode current? What is the peak reverse voltage across each diode? Specify the diode in terms of its peak current and its PIV.

Ans. 1281  $\mu\text{F}$ ; 15.4 V or (a better estimate) 14.9 V; 0.15 A; 0.36 rad (20.7°); 1.45 A; 2.74 A; 16.2 V. Thus select a diode with 3.5 A to 4 A peak current and a 20-V PIV rating.


Dr. D. M. Akbar Hussain

Copyright © 2004 by Oxford University Press, Inc.

Department of Electronic Systems

25

## Super Diode (Precision Half Wave Rectifier)

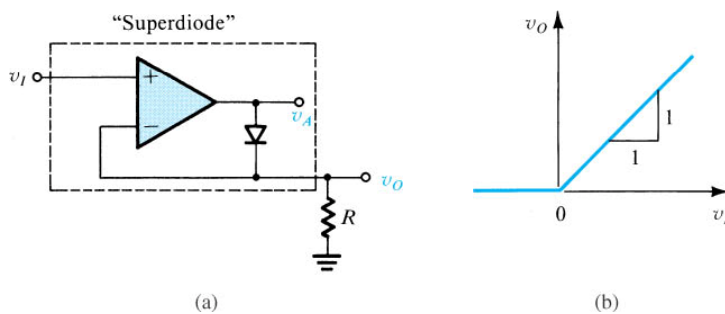

**Figure 3.31** The “superdiode” precision half-wave rectifier and its almost-ideal transfer characteristic. Note that when  $v_I > 0$  and the diode conducts, the op amp supplies the load current, and the source is conveniently buffered, an added advantage. Not shown are the op-amp power supplies.


Dr. D. M. Akbar Hussain

Copyright © 2004 by Oxford University Press, Inc.

Department of Electronic Systems

26

## Exercise 3.25 & 3.26

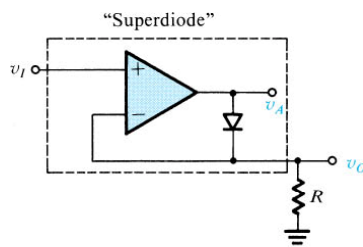

(a)

### EXERCISES

3.25 Consider the operational rectifier or superdiode circuit of Fig. 3.31(a), with  $R = 1 \text{ k}\Omega$ . For  $v_I = 10 \text{ mV}$ ,  $1 \text{ V}$ , and  $-1 \text{ V}$ , what are the voltages that result at the rectifier output and at the output of the op amp? Assume that the op amp is ideal and that its output saturates at  $\pm 12 \text{ V}$ . The diode has a  $0.7\text{-V}$  drop at  $1\text{-mA}$  current, and the voltage drop changes by  $0.1 \text{ V}$  per decade of current change.

Ans.  $10 \text{ mV}$ ,  $0.51 \text{ V}$ ;  $1 \text{ V}$ ,  $1.7 \text{ V}$ ;  $0 \text{ V}$ ,  $-12 \text{ V}$

3.26 If the diode in the circuit of Fig. 3.31(a) is reversed, find the transfer characteristic  $v_O$  as a function of  $v_I$ .

Ans.  $v_O = 0$  for  $v_I \geq 0$ ;  $v_O = v_I$  for  $v_I \leq 0$

Dr. D. M. Akbar Hussain

Copyright © 2004 by Oxford University Press, Inc.

Department of Electronic Systems

27

## Limiting & Clamping Circuits

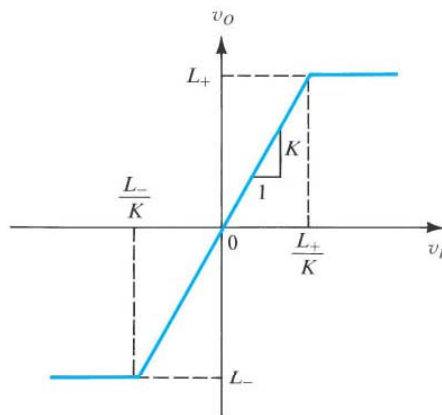


Figure 3.32 General transfer characteristic for a limiter circuit.

Dr. D. M. Akbar Hussain

Copyright © 2004 by Oxford University Press, Inc.

Department of Electronic Systems

28

## Clipper

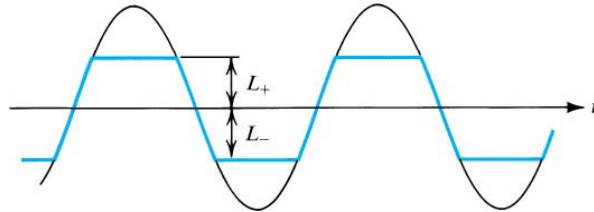



Figure 3.33 Applying a sine wave to a limiter can result in clipping off its two peaks.

Copyright © 2004 by Oxford University Press, Inc.

Dr. D. M. Akbar Hussain  
Department of Electronic Systems

29

## Soft Limiter

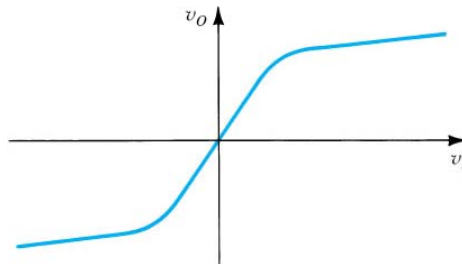

Copyright © 2004 by Oxford University Press, Inc.

Dr. D. M. Akbar Hussain  
Department of Electronic Systems

30

## Basic Limiting Circuits

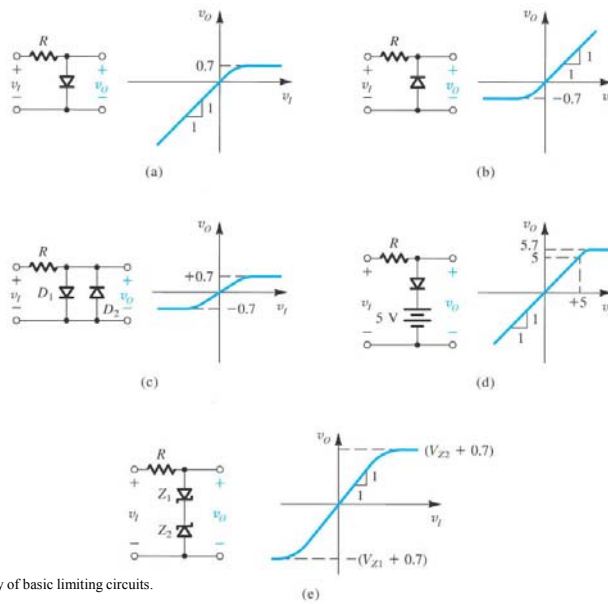


Figure 3.35 A variety of basic limiting circuits.

Dr. D. M. Akbar Hussain

## Exercise 3.27



### EXERCISE

3.27 Assuming the diodes to be ideal, describe the transfer characteristic of the circuit shown in Fig. E3.27.

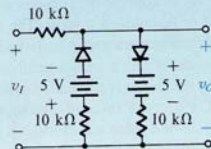



FIGURE E3.27

Ans.  $v_o = v_i$  for  $-5 \leq v_i \leq +5$   
 $v_o = \frac{1}{2}v_i - 2.5$  for  $v_i \leq -5$   
 $v_o = \frac{1}{2}v_i + 2.5$  for  $v_i \geq +5$

Dr. D. M. Akbar Hussain




## Clamped Capacitor/ DC Restorer

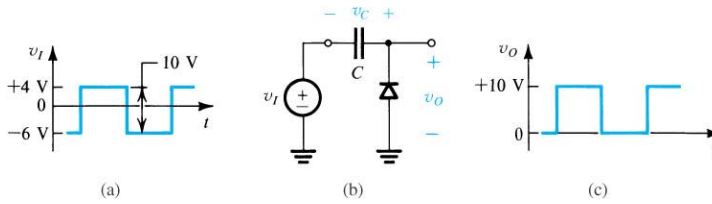

Copyright © 2004 by Oxford University Press, Inc. **Dr. D. M. Akbar Hussain**  
 Department of Electronic Systems

33


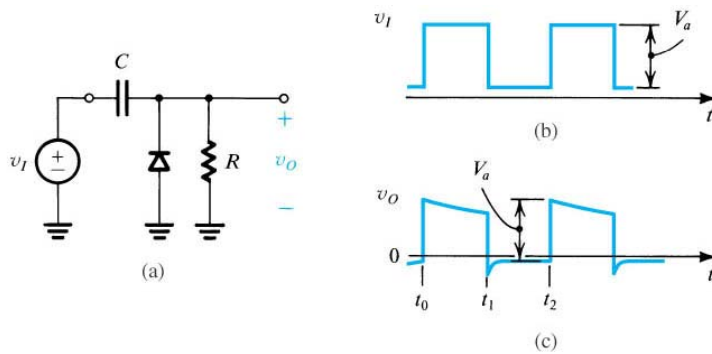
## Clamped Capacitor with a Load Resistor



Copyright © 2004 by Oxford University Press, Inc. **Dr. D. M. Akbar Hussain**  
 Department of Electronic Systems

34

## Volatge Doubler

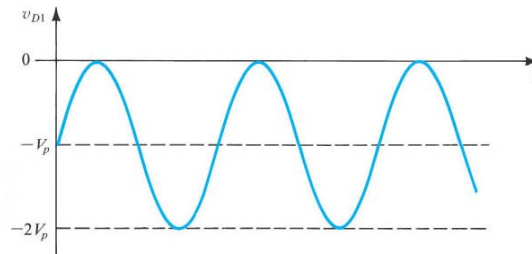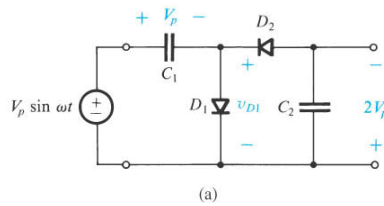


Dr. D. M. Akbar Hussain

Copyright © 2004 by Oxford University Press, Inc.

Department of Electronic Systems

35

## Exercise 3.28

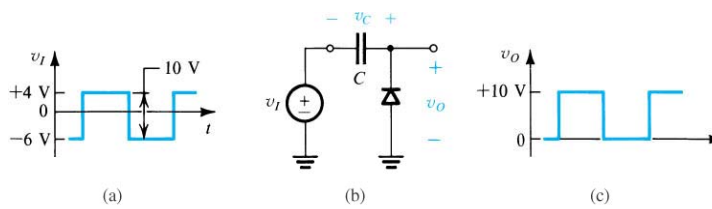

### EXERCISE

3.28 If the diode in the circuit of Fig. 3.36 is reversed, what will the dc component of  $v_o$  become?  
 Ans.  $-5$  V


Dr. D. M. Akbar Hussain

Copyright © 2004 by Oxford University Press, Inc.

Department of Electronic Systems

36
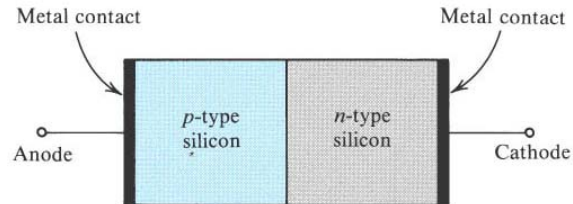
## Physical Structure of the Junction Diode




Dr. D. M. Akbar Hussain

Copyright © 2004 by Oxford University Press, Inc.

Department of Electronic Systems

37

## Silicon Crystal at Low Temperature

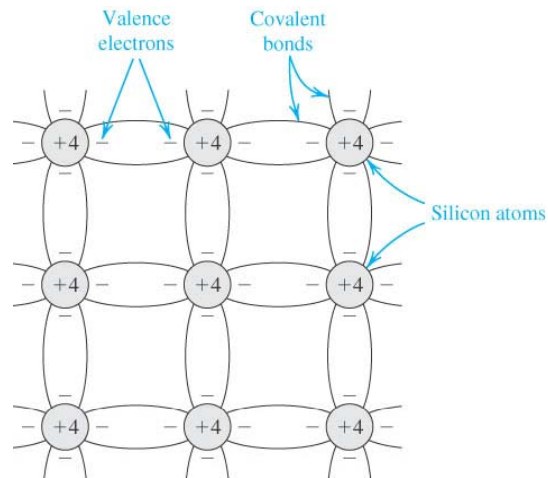

**Figure 3.40** Two-dimensional representation of the silicon crystal. The circles represent the inner core of silicon atoms, with +4 indicating its positive charge of +4q, which is neutralized by the charge of the four valence electrons. Observe how the covalent bonds are formed by sharing of the valence electrons. At 0 K, all bonds are intact and no free electrons are available for current conduction.


Dr. D. M. Akbar Hussain

Copyright © 2004 by Oxford University Press, Inc.

Department of Electronic Systems

38

## Silicon Crystal at Room Temperature

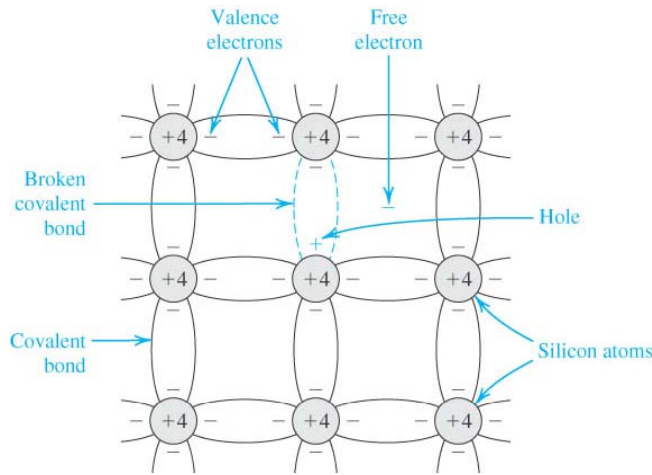

**Figure 3.41** At room temperature, some of the covalent bonds are broken by thermal ionization. Each broken bond gives rise to a free electron and a hole, both of which become available for current conduction.


**Dr. D. M. Akbar Hussain**

Copyright © 2004 by Oxford University Press, Inc.

**Department of Electronic Systems**

39

## Drift & Diffusion

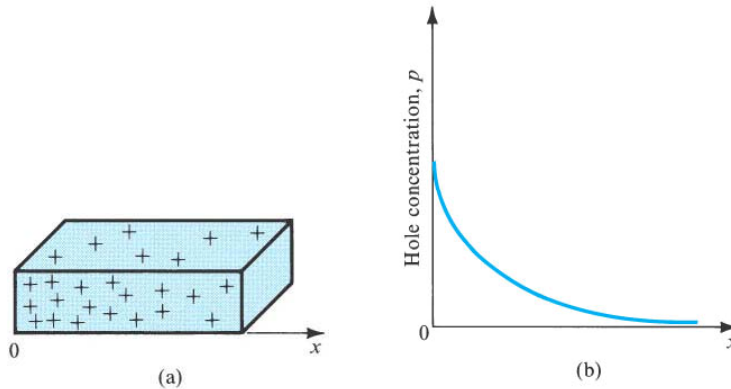

$$J_p = -qD_p \frac{dp}{dx}$$

$$v_{drift} = \mu_p E$$

$$J_{p-drift} = qp\mu_p E$$

$$J_{n-drift} = qp\mu_n E$$

**Figure 3.42** A bar of intrinsic silicon (a) in which the hole concentration profile shown in (b) has been created along the x-axis by some unspecified mechanism.


**Dr. D. M. Akbar Hussain**

Copyright © 2004 by Oxford University Press, Inc.

**Department of Electronic Systems**

40

## Doped Semiconductor (n-type)

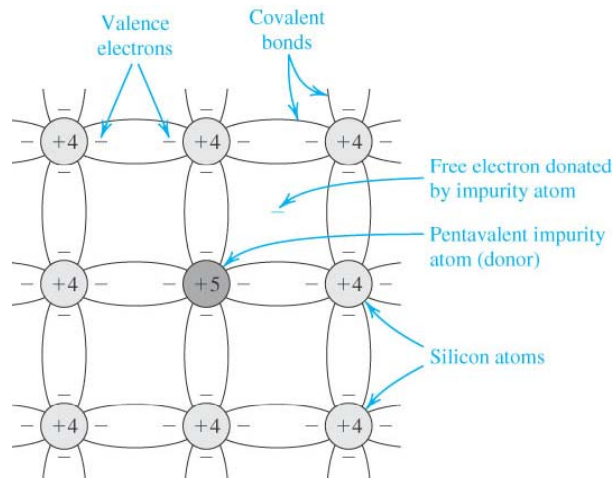

**Figure 3.43** A silicon crystal doped by a pentavalent element. Each dopant atom donates a free electron and is thus called a donor. The doped semiconductor becomes *n* type.


**Dr. D. M. Akbar Hussain**

Copyright © 2004 by Oxford University Press, Inc.

**Department of Electronic Systems**

41

## Doped Semiconductor (p-type)

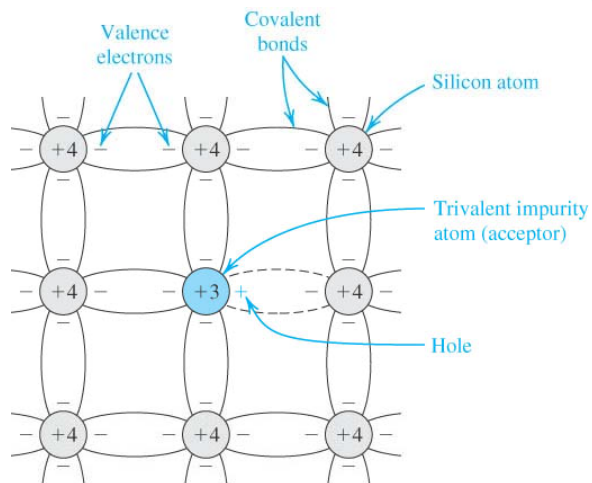

**Figure 3.44** A silicon crystal doped with a trivalent impurity. Each dopant atom gives rise to a hole, and the semiconductor becomes *p* type.

**Dr. D. M. Akbar Hussain**

Copyright © 2004 by Oxford University Press, Inc.

**Department of Electronic Systems**

42

## pn Junction Under Open Circuit Condition

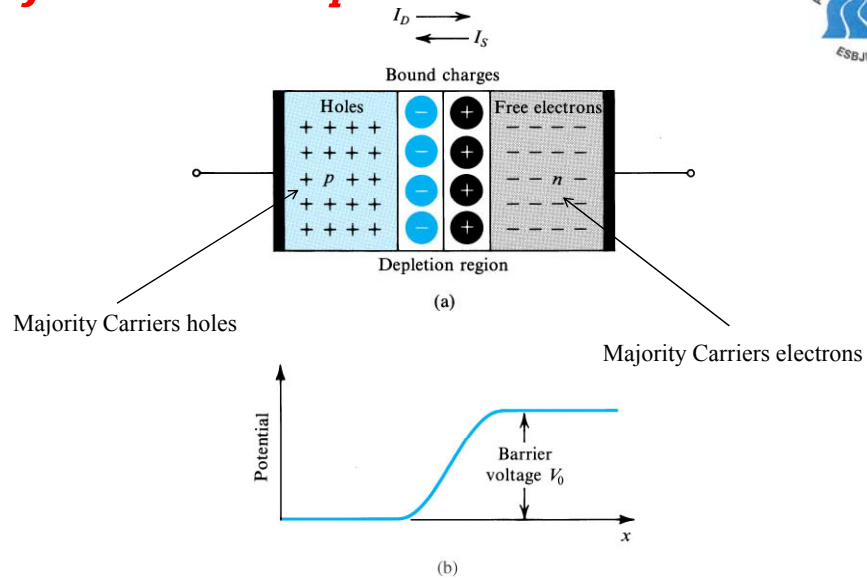


Figure 3.45 (a) The *pn* junction with no applied voltage (open-circuited terminals). (b) The potential distribution along an axis perpendicular to the junction.

Dr. D. M. Akbar Hussain

Copyright © 2004 by Oxford University Press, Inc.

Department of Electronic Systems

43

## pn Junction Under Reverse Bias Condition

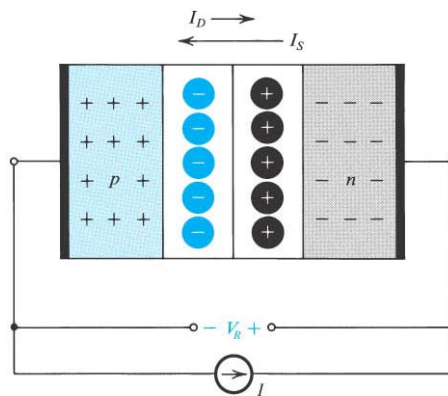


Figure 3.46 The *pn* junction excited by a constant-current source  $I$  in the reverse direction. To avoid breakdown,  $I$  is kept smaller than  $I_S$ . Note that the depletion layer widens and the barrier voltage increases by  $V_R$  volts, which appears between the terminals as a reverse voltage.

Dr. D. M. Akbar Hussain

Copyright © 2004 by Oxford University Press, Inc.

Department of Electronic Systems

44

## Depletion Capacitance

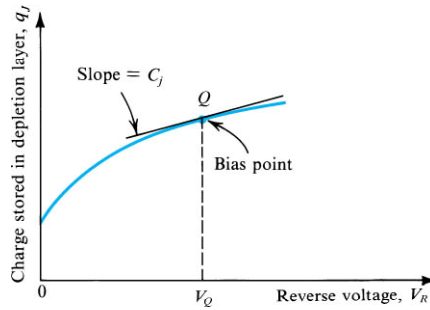


Figure 3.47 The charge stored on either side of the depletion layer as a function of the reverse voltage  $V_R$ .

Dr. D. M. Akbar Hussain

Copyright © 2004 by Oxford University Press, Inc.

Department of Electronic Systems

45

## pn Junction in Breakdown Region

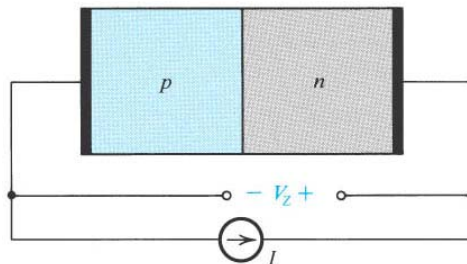


Figure 3.48 The  $pn$  junction excited by a reverse-current source  $I$ , where  $I > I_S$ . The junction breaks down, and a voltage  $V_Z$ , with the polarity indicated, develops across the junction.


Dr. D. M. Akbar Hussain

Copyright © 2004 by Oxford University Press, Inc.

Department of Electronic Systems

46

## Pn Junction Under Forward Bias Condition

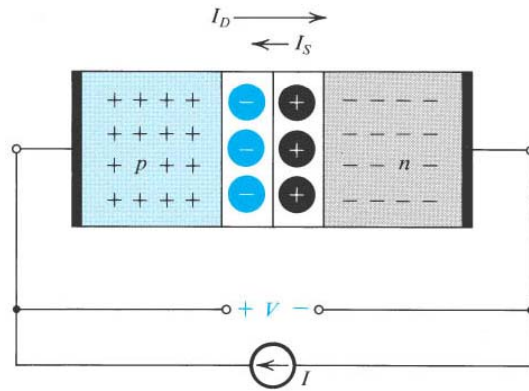

**Figure 3.49** The  $pn$  junction excited by a constant-current source supplying a current  $I$  in the forward direction. The depletion layer narrows and the barrier voltage decreases by  $V$  volts, which appears as an external voltage in the forward direction.


**Dr. D. M. Akbar Hussain**

Copyright © 2004 by Oxford University Press, Inc.

**Department of Electronic Systems**

47

## Minority Carrier Distribution

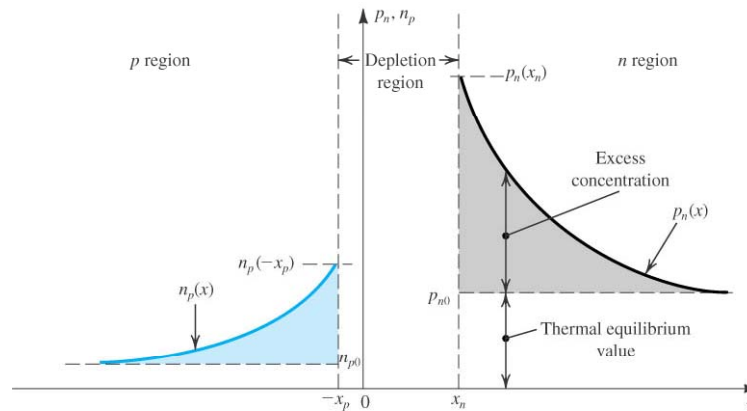

**Figure 3.50** Minority-carrier distribution in a forward-biased  $pn$  junction. It is assumed that the  $p$  region is more heavily doped than the  $n$  region;  $N_A \gg N_D$ .

**Dr. D. M. Akbar Hussain**

Copyright © 2004 by Oxford University Press, Inc.

**Department of Electronic Systems**

48



## ***Special Diodes***



- ***Schottky Barrier Diode (SBD)***
- ***Varactors***
- ***Photo-Diodes***
- ***Light Emitting Diodes***

## ***Home work:***

***Problems: 3.11, 3.12, 3.13, 3.14, 3.15,  
3.16, 3.66, 3.67, 3.77, 3.78***

